
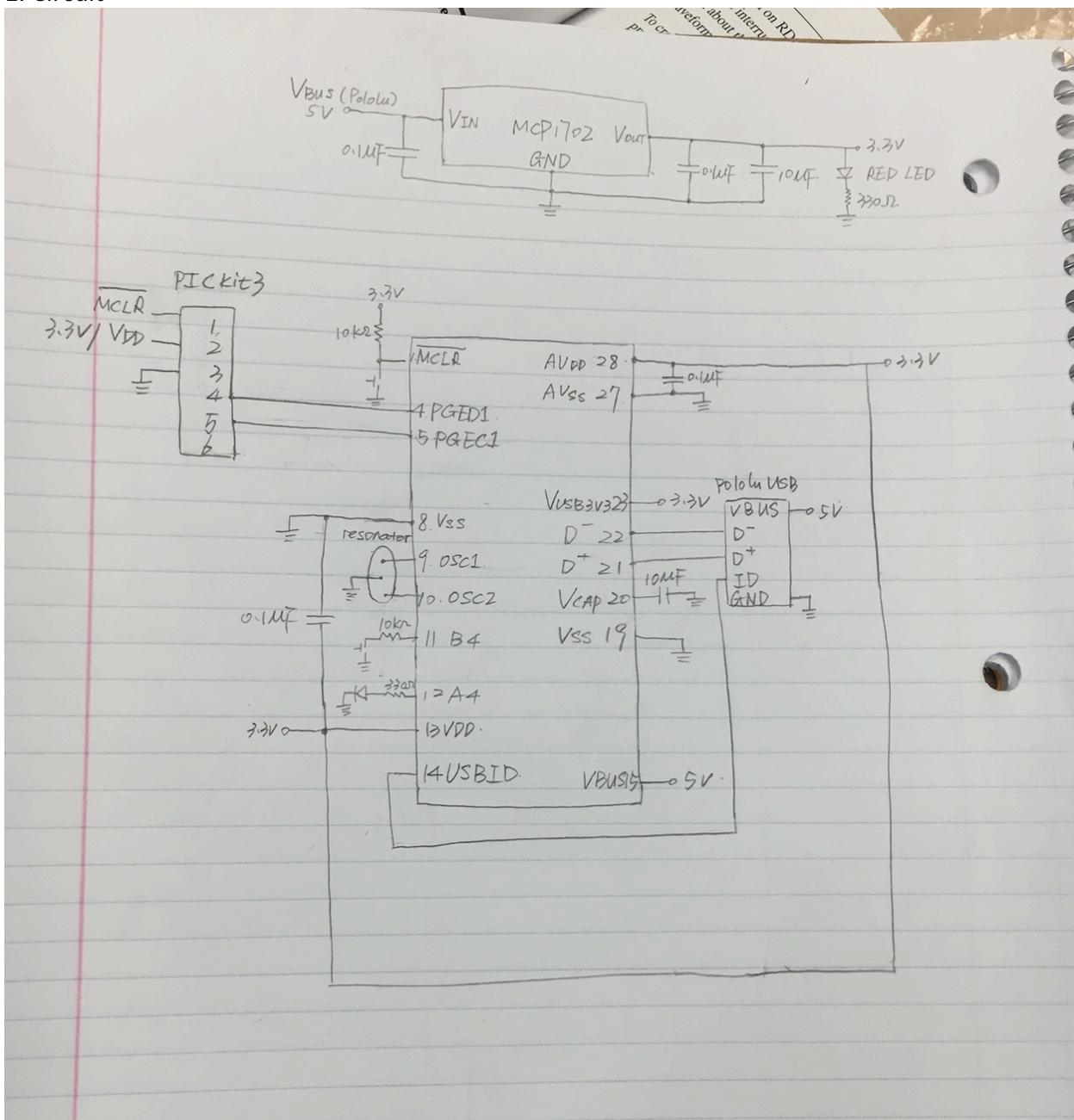


Wanning Zhu HW1


1. Circuit

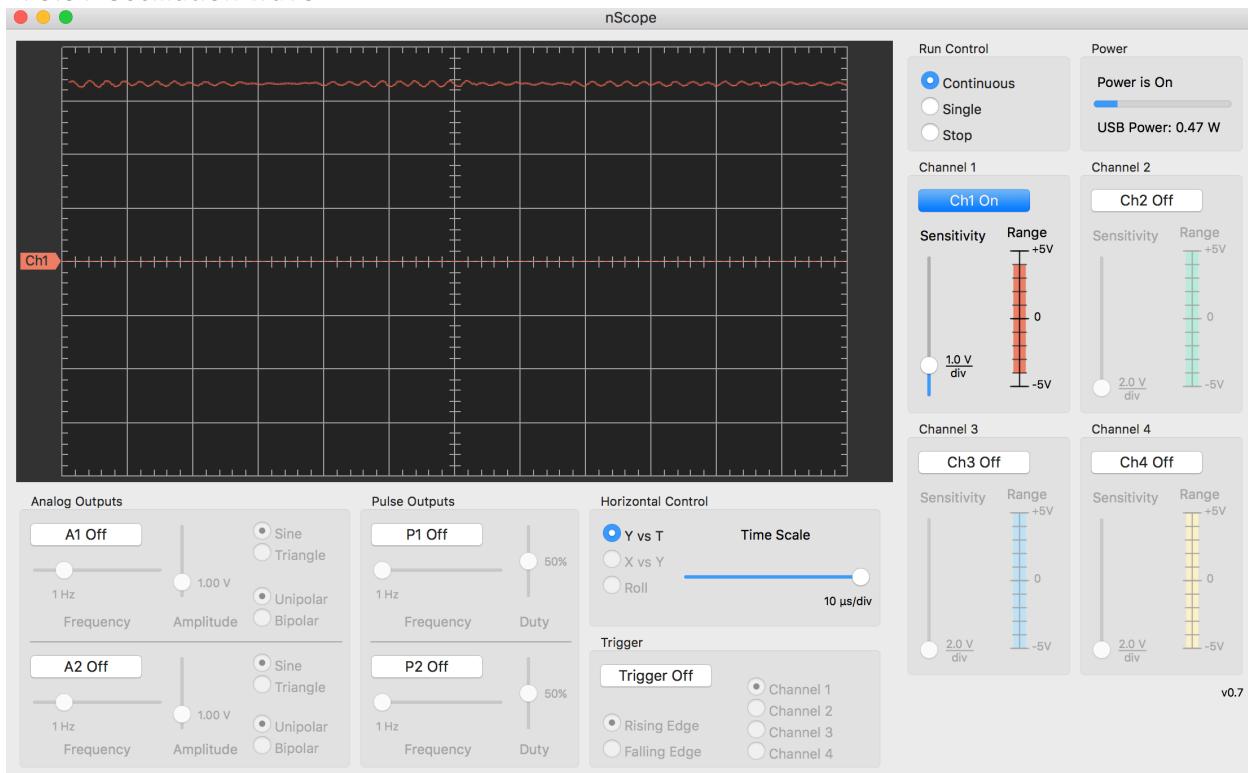

2. 3.3V Oscillation wave



3. 3.3V Clean wave

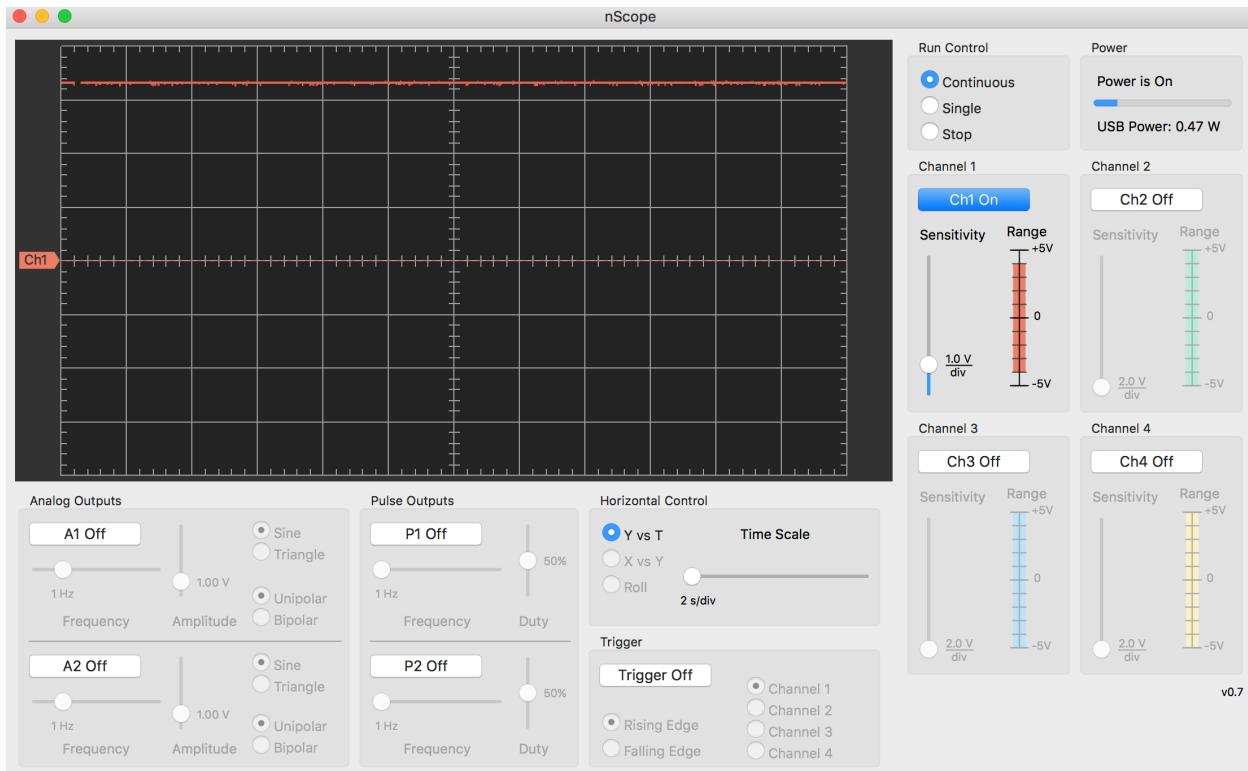

4. Breadboard

